
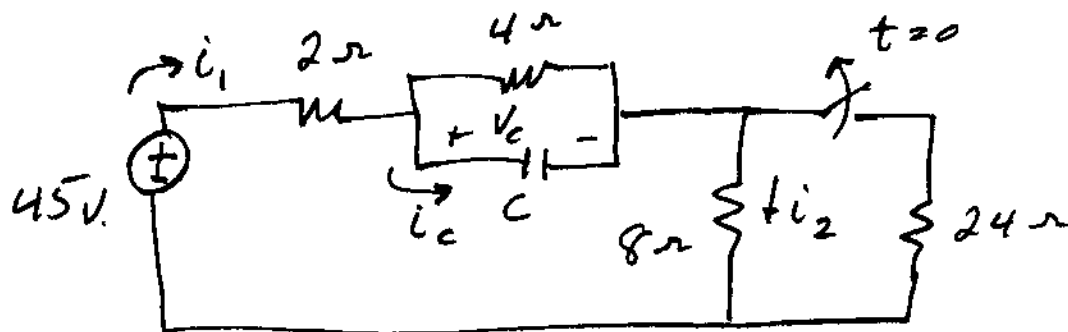


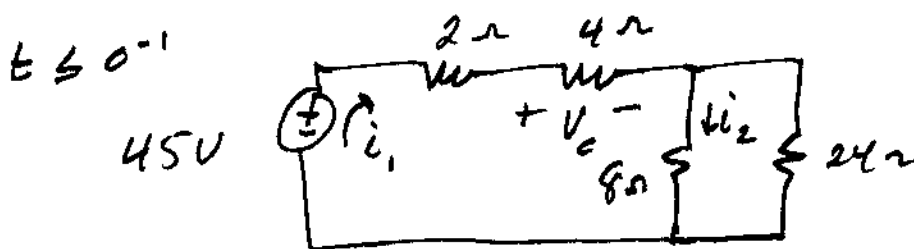1. If $i_1(0^-) = \frac{15}{4} A$ Find i_1, i_2, i_c and V_c at $t=0^+$



Verify the $t=0^-$ condition



$$R_1 = \frac{8(24)}{32} = 6 \Omega$$


$$i_1 = \frac{45}{12} = \frac{15}{4} A$$

$$i_2(0^-) = \frac{24}{32} \left[\frac{15}{4} \right]$$

$$i_2(0^-) = 2.8125 A$$

$$V_c(0^-) = 4 \left(\frac{15}{4} \right)$$

$$V_c(0^-) = 15 V$$

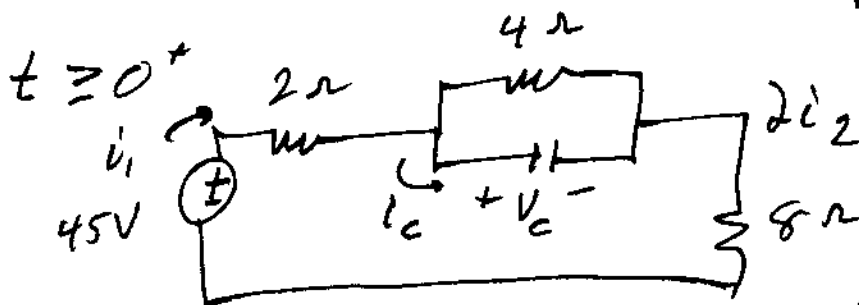

$$V_c(0^+) = 15 V$$

$$i_{4\Omega}(0^+) = \frac{15}{4} A$$


$$-45 + 2i_1 + V_c + 8i_1 = 0$$

$$10i_1 = 45 - 15$$

$$i_1(0^+) = 3 A = i_2(0^+)$$


$$i_c(0^+) = 3 - \frac{15}{4} = -\frac{3}{4} A$$

2.

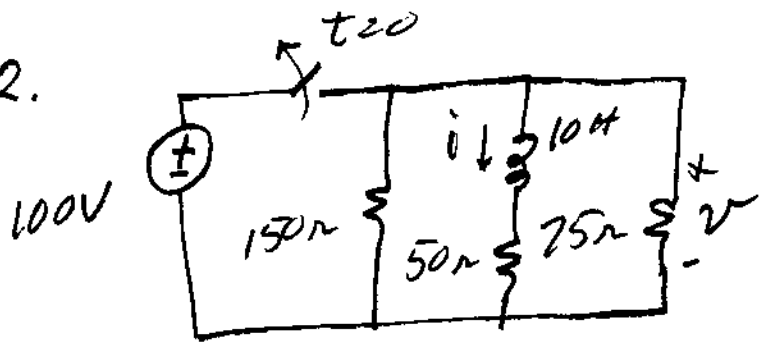


DC steady state
at $t = 0^-$
Verify that
 $i(0^-) = 2A$

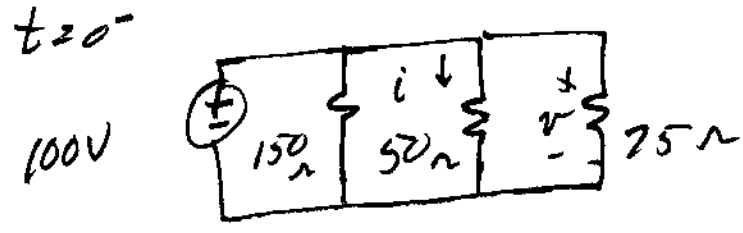Find the complete response for v , $t > 0$.



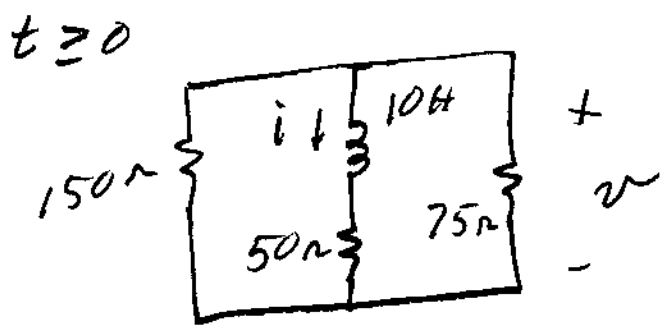$i(0^-) = \frac{100}{50} = 2A$
 $i(0^-) = i(0^+) = 2A$



R_{eq} as seen by
the 10H
inductor.

$$R_{eq} = 50 + \frac{75(150)}{75+150} = 100 \Omega$$


$$\tau = \frac{L}{R_{eq}} = .1 s$$

$$i(t) = 2e^{-10t} A$$



$$v(t) = 10 \frac{di}{dt} + 50i = 10[-20e^{-10t}] + 100e^{-10t}$$

$$v(t) = -100e^{-10t} V.$$

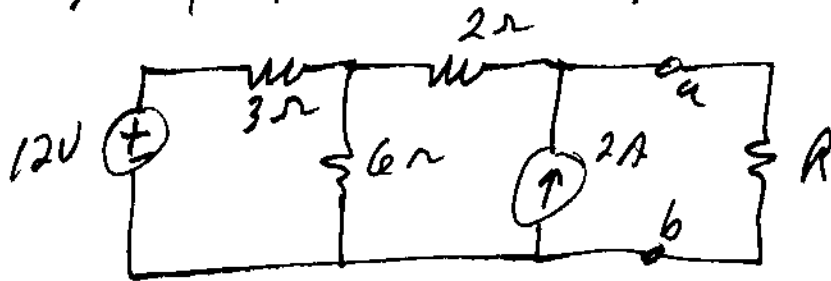3. (a) Find the value of R that yields the $\frac{1}{3}$ max Power Transfer.



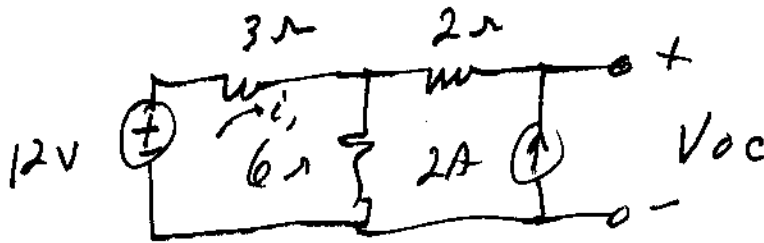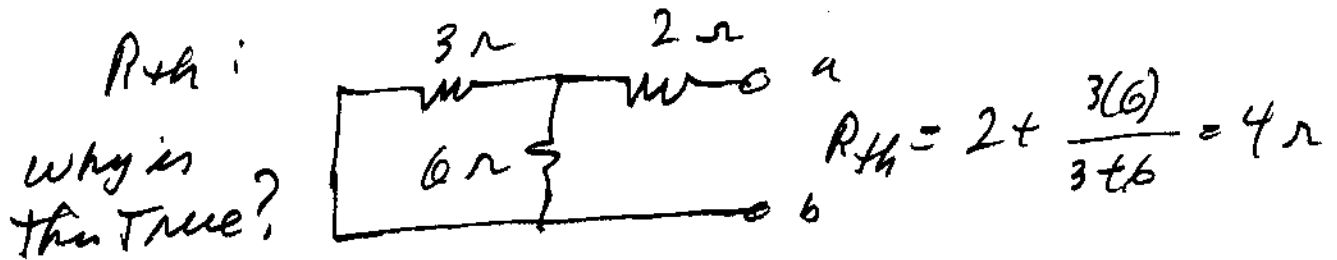a) Find Thevenin & Norton Equivalent circuit.




$$-12 + 9i_1 + 6(2) = 0$$

$$9i_1 = 12 - 12 = 0 \Rightarrow i_1 = 0 \text{ A}$$


$$0.6 + 8(2) - V_{oc} = 0$$

$$V_{oc} = 16 \text{ VOLTS}$$
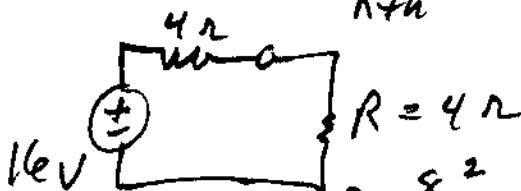
$$I_{sc} = \frac{V_{oc}}{R_{th}} = \frac{16}{4} = 4 \text{ A}$$








$$P = \frac{8^2}{4} = 16 \text{ W}$$

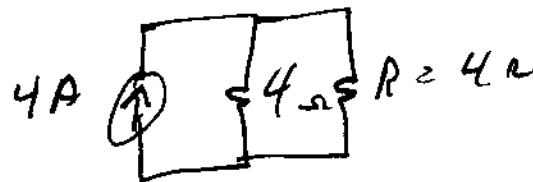


$$P = (2)^2 \cdot 4 = 16 \text{ W}$$

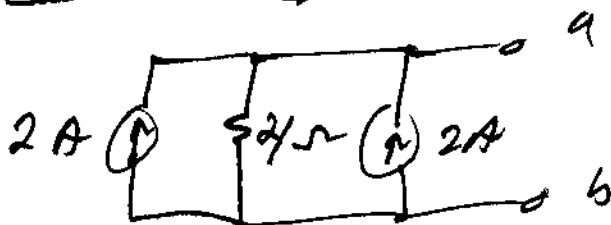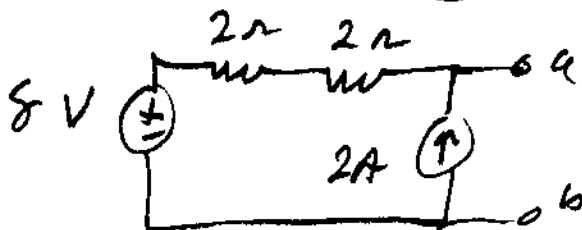
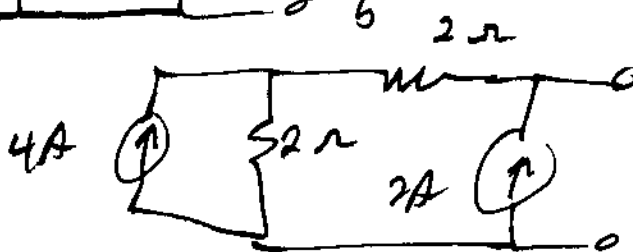
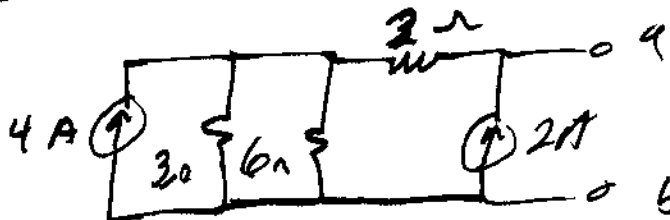
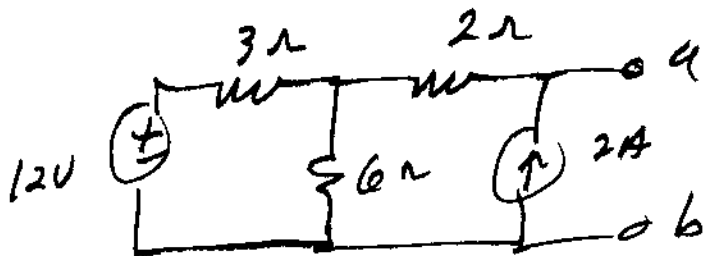
3 cont Find Thevenin & Norton equivalents using Source Trans. 2/3




NORTON

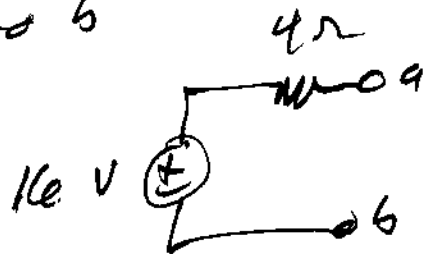

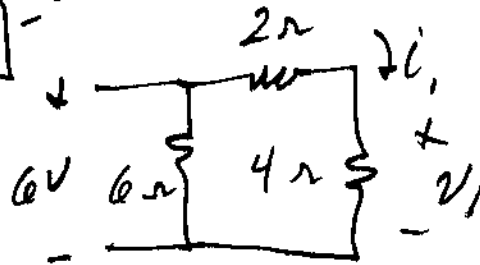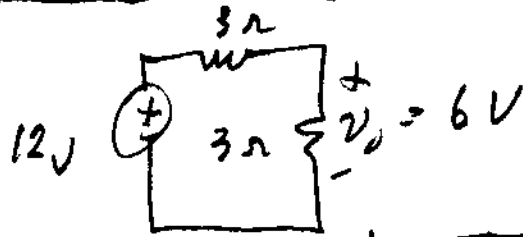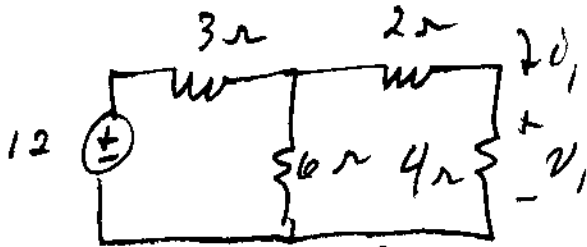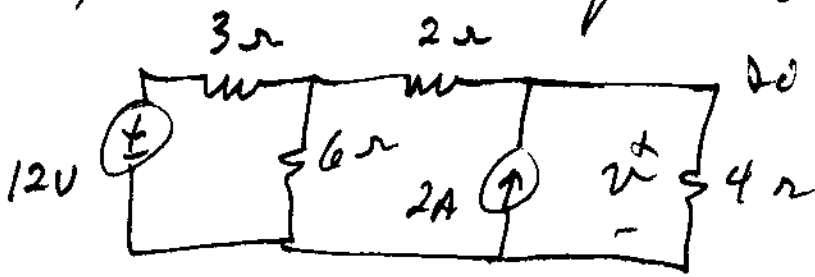
3 cont Let $R = 4\Omega$ Use superposition to find i and v 3/3


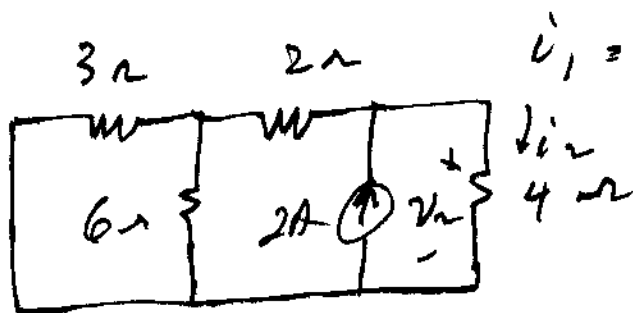
$$\Rightarrow v_1 = \frac{4}{6}(6) = 4V$$



$$i_1 = \frac{4}{4} = 1A$$

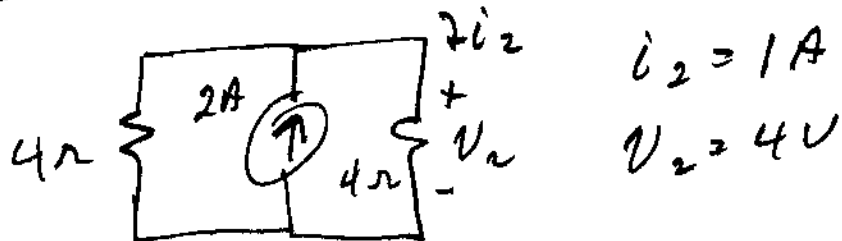


$$i_2 = 1A$$

$$v_2 = 4V$$

$$i = i_1 + i_2 = 1 + 1 = 2A$$

$$v = 4 + 4 = 8V$$

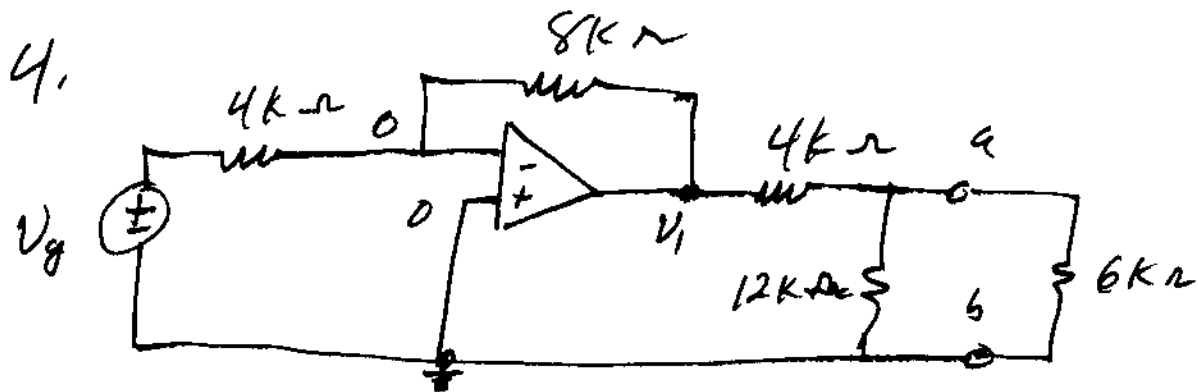

$V_g = 6 \cos 2t \text{ V}$ Find the Norton eq. chpt
to the left of ports a, b
Use the results to find the power
delivered to the $6 \text{ k}\Omega$ resistor.

$$\frac{0 - V_g}{4\text{k}} + \frac{0 - V_1}{8\text{k}} = 0 \Rightarrow \frac{V_1}{8} = -\frac{V_g}{4}$$

$$V_1 = -2V_g$$

$$V_{oc} = \frac{12}{16} V_1 = \frac{3}{4} [-2V_g] = -\frac{3}{2} V_g$$

$$V_{oc} = -9 \cos 2t \text{ V.}$$

$$i_{sc} = \frac{V_1}{4\text{k}} = -\frac{1}{2} V_g \text{ mA} = -3 \cos 2t \text{ mA}$$


$$R_{th} = \frac{V_{oc}}{i_{sc}} = \frac{-9 \cos 2t \text{ V}}{-3 \cos 2t \text{ mA}} = 3 \text{ k}\Omega$$

$$P = (6000) \left(\frac{3\text{k}}{3\text{k} + 6\text{k}} i_{sc} \right)^2 = 6 \left[\frac{3}{9} (-3 \cos 2t) \right]^2 \times 10^{-3}$$

$$P = 6 \cos^2 2t \text{ mW}$$

5. Given

1/4

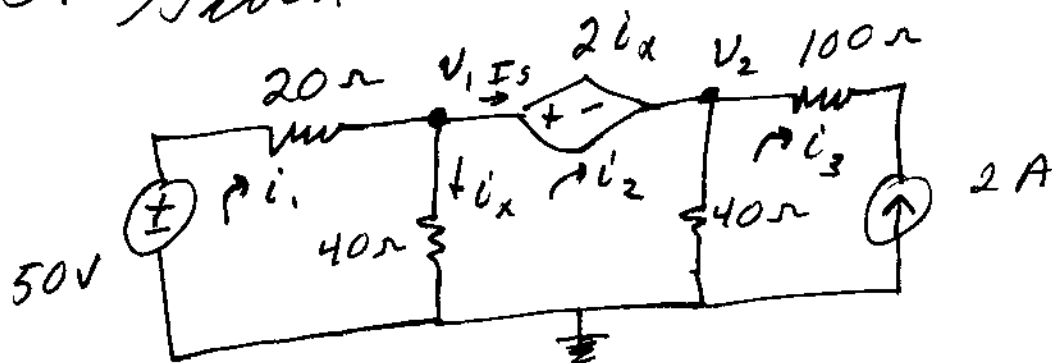

a) use Nodal analysis to find V_1, V_2

i) "Super Node - eliminate I_s "

ii) include I_s

$$\textcircled{1} \quad \frac{V_1 - 50}{20} + \frac{V_1}{40} + I_s = 0$$

Dependency eq

$$i_x = \frac{V_1}{40}$$

$$\textcircled{2} \quad -I_s + \frac{V_2}{40} - 2 = 0$$

add these
eliminate I_s

$$\frac{V_1 - 50}{20} + \frac{V_1}{40} + \frac{V_2}{40} - 2 = 0$$

"super node"

$$3V_1 + V_2 = 180$$

CONSTRAINT EQUATION:

$$-V_1 + 2i_x + V_2 = 0$$

$$-V_1 + 2\left(\frac{V_1}{40}\right) + V_2 = 0$$

$$-19V_1 + 20V_2 = 0$$

5a
cont

2 equations 2 unknowns.

$$3V_1 + V_2 = 180$$

$$-19V_1 + 20V_2 = 0$$

$$\begin{bmatrix} 3 & 1 \\ -19 & 20 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 180 \\ 0 \end{bmatrix}$$

$$\Rightarrow V_1 = 45.57 \text{ V}$$

$$V_2 = +43.29 \text{ V}$$

$$I_x = \frac{45.57}{40} = 1.14 \text{ A}$$

$$-I_s + \frac{43.24}{40} - 2 = 0 \Rightarrow I_s = -.9128 \text{ A}$$

5a cont Nodal Analysis with I_s

3/4

$$\textcircled{1} \quad \frac{V_1 - 50}{20} + \frac{V_1}{40} + I_s = 0$$

$$3V_1 + 40I_s = 100$$

$$\textcircled{2} \quad -I_s + \frac{V_2}{40} - 2 = 0$$

$$V_2 - 40I_s = 80$$

$$\textcircled{3} \text{ constraint eq } -19V_1 + 20V_2 = 0$$


$$\begin{bmatrix} 3 & 0 & 40 \\ 0 & 1 & -40 \\ -19 & 20 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ I_s \end{bmatrix} = \begin{bmatrix} 100 \\ 80 \\ 0 \end{bmatrix}$$

$$V_1 = 45.57 \text{ V}$$

$$V_2 = 43.29 \text{ V}$$

$$I_s = -0.1978$$

MESH ANALYSIS

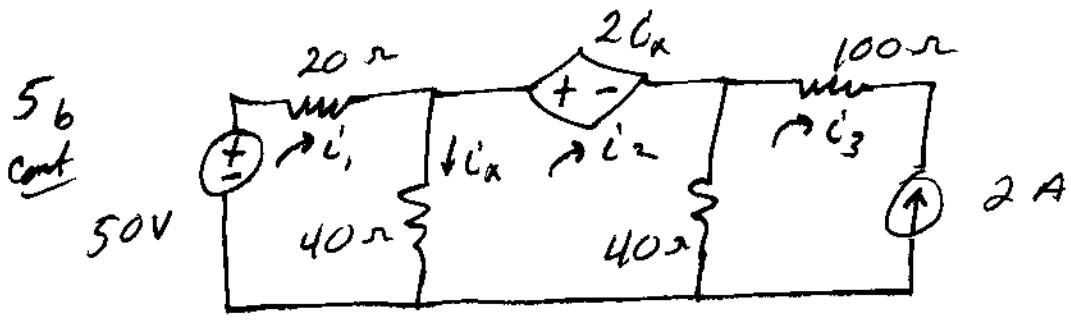

$$i_3 = -2A$$

Dependency eq: $i_x = i_1 - i_2$

$$\begin{aligned} \textcircled{1} \quad & -50 + 60i_1 - 40i_2 = 0 \\ & 60i_1 - 40i_2 = 50 \end{aligned}$$

$$\begin{aligned} \textcircled{2} \quad & -40i_1 + 2[i_1 - i_2] + 80i_2 = 80 \quad \text{NOTE } [i_1 - i_2] = i_x \\ & -38i_1 + 78i_2 = -80 \end{aligned}$$


$$\begin{bmatrix} 60 & -40 \\ -38 & 78 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 50 \\ -80 \end{bmatrix}$$

$$i_1 = .222 A$$

$$i_2 = -.918 A$$

$$i_x = i_1 - i_2 = 1.14$$

6.

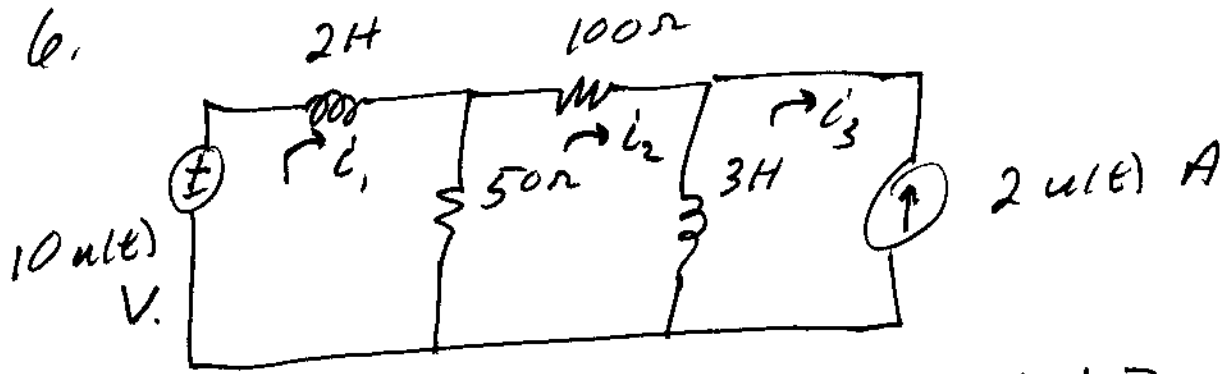

$$i_3 = -2A \quad t \geq 0$$


Find $i_1(t)$, $t \geq 0$ Complete Sol.

Need to determine:

- $i_1(0)$
- FORM OF THE NATURAL RESPONSE
 $s_1, s_2 \Rightarrow ?$ [TWO CONSTANTS] A_1, A_2
- Forced Response
- $\frac{di_1(0^+)}{dt}$
- Then solve for A_1, A_2
- Then you have the complete solution.

6.

2/6

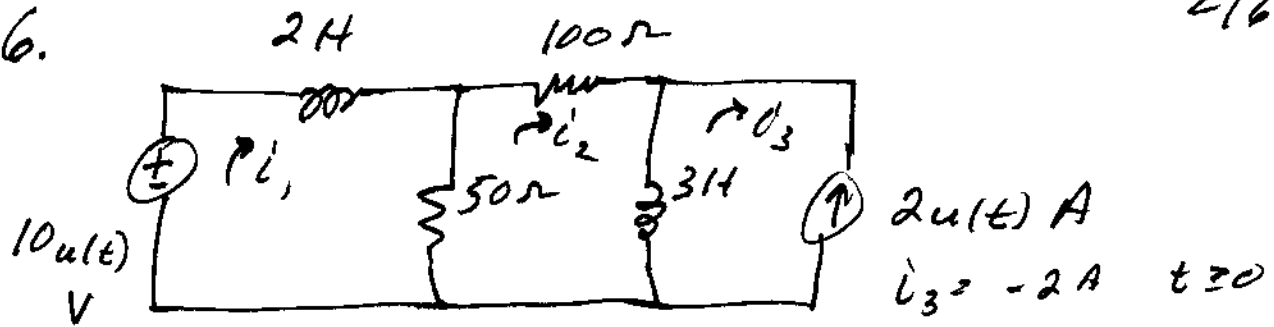

Find $i_1(t)$, $t \geq 0$ Complete solution

Use Mesh analysis all i.c are zero

$$\textcircled{1} \quad -10 + 2 \frac{di_1}{dt} + 50(i_1 - i_2) = 0$$

$$2 \frac{di_1}{dt} + 50i_1 - 50i_2 = 0$$

$$\textcircled{2} \quad -50i_1 + 150i_2 + 3 \frac{d(i_2 - (-2))}{dt} = 0$$

$$3 \frac{di_2}{dt} + 150i_2 - 50i_1 = 0$$

$$s \equiv \frac{d}{dt}$$

$$\textcircled{1} \quad 2s i_1 + 50i_1 - 50i_2 = 10$$

$$(2s + 50)i_1 - 50i_2 = 10$$

$$\textcircled{2} \quad 3s i_2 - 150i_2 - 50i_1 = 0$$

$$-50i_1 + (3s + 150)i_2 = 0$$

Cont

3/6

$$i_1 = \frac{\begin{vmatrix} 10 & -50 \\ 0 & (35+150) \end{vmatrix}}{\begin{vmatrix} (25+50) & -50 \\ -50 & (35+150) \end{vmatrix}}$$

$$= \frac{10(35+150)}{(25+50)(35+150) - (-50)(-50)}$$

$$= \frac{10(35+150)}{6s^2 + 300s + 150s + 7500 - 2500}$$

$$= \frac{10(35+150)}{6s^2 + 450s + 5000} = \frac{10(35+150)}{s^2 + 75s + 833.3}$$

$$s_{1,2} = \frac{-75 \pm \sqrt{75^2 - 4(833.3)}}{2}$$


$$s_1 = -85.37 \quad s_2 = -10.37$$

$$i_1(t) = A_1 e^{-85.37t} + A_2 e^{-10.37t} + i_f$$

over damped

6 cont The initial conditions were all zero 4/6
 $i_1(0) = 0$

Forced Response:

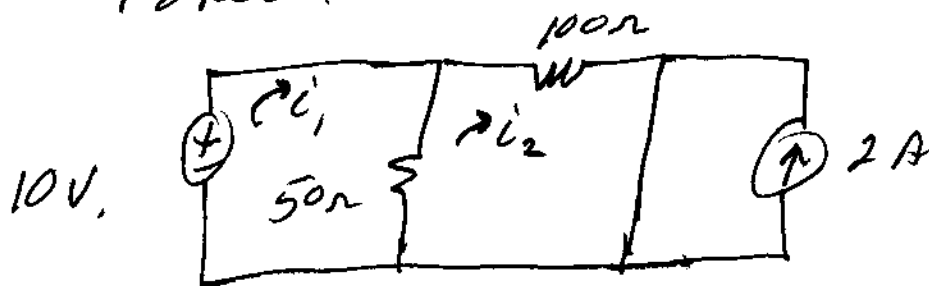

$$\textcircled{1} \quad -10 + 50i_1 - 50i_2 = 0$$

$$50i_1 - 50i_2 = 10$$

$$\textcircled{2} \quad -50i_1 + 150i_2 = 0 \quad \text{--- why?}$$

$$\Rightarrow 100i_2 = 10$$

$$i_2 = \frac{10}{100} = .1 \text{ A}$$

$$50i_1 = 10 + 50(.1)$$

$$i_1 = \frac{15}{50} = .3 \text{ A}$$


\Rightarrow

$$i_1(t) = A_1 e^{-85.37t} + A_2 e^{-10.37t} + .3 \quad \text{A}$$

$$t \geq 0$$

6) $t = 0^+$

5/6

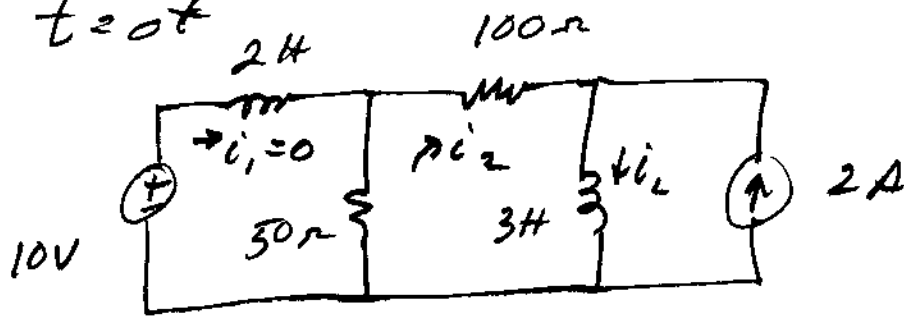

$$i_1(0^-) = i_1(0^+) = 0$$

$$i_L(0^-) = i_L(0^+) = 0$$

$$0 = i_2 + 2$$

$$\Rightarrow i_2 = -2 \text{ A}$$

$$-10 + 2 \frac{di_1(0^+)}{dt} + 50(0 - (-2)) = 0$$

$$\begin{aligned} 2 \frac{di_1(0^+)}{dt} &= 10 - 50(0 - (-2)) = 10 - 50(2) \\ &= 10 - 100 = -90 \end{aligned}$$

$$\frac{di_1(0^+)}{dt} = -45 \text{ A/s}$$

6 cont

6/6

$$\frac{di_1}{dt} = -85.37A_1 e^{-85.37t} - 10.37A_2 e^{-10.37t} + 0$$

↑
since
forced
response
is
constant

$$\frac{di_1(0^+)}{dt} = -45 = -85.37A_1 - 10.37A_2$$

$$i_1(0) = 0 = A_1 + A_2 + .3$$

$$\begin{bmatrix} -85.37 & -10.37 \\ 1 & 1 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} -45 \\ -.3 \end{bmatrix}$$

$$A_1 = .6415$$

$$A_2 = -.9418$$

$$i_1(t) = .6415 e^{-85.37t} - .9418 e^{-10.37t} + .3 \text{ u(t) A}$$